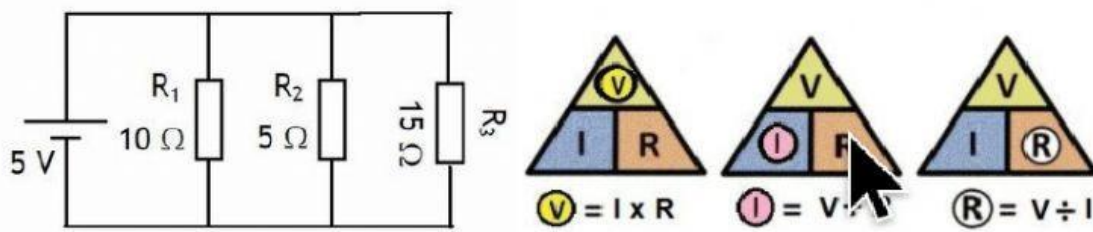


1. Resol el circuit:



	R_1	R_2	R_3	total
R				
V				
I				