
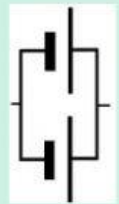
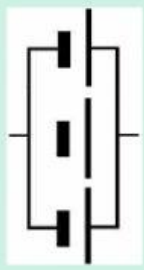
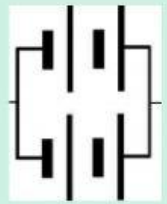



전압

1. 1.5V 전지를 다양한 방법(직렬, 병렬, 혼합)으로 연결하였을 때, 각각의 전압의 크기는?

				
() V	() V	() V	() V	() V

2. 전기 회로에 알맞은 전기 회로도를 완성하시오.

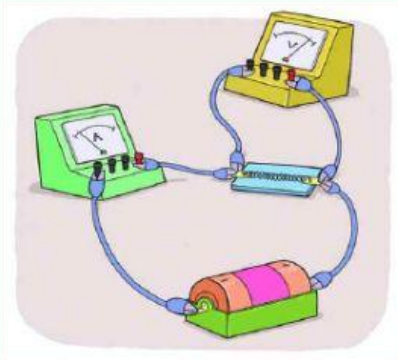

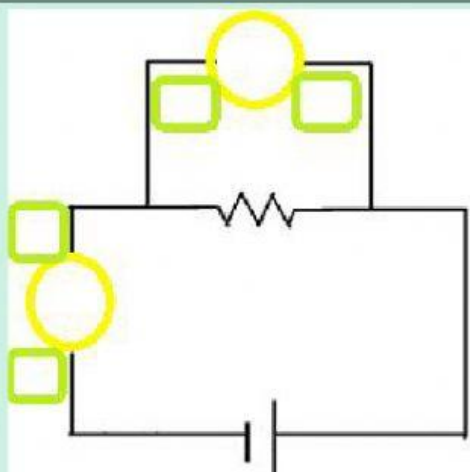


(보기)


 (+)
 (-)


 (+)
 (-)

3. 각각의 전압계에 표시된 눈금을 보고, 알맞은 전압의 세기에 해당되는 것을 고르시오.

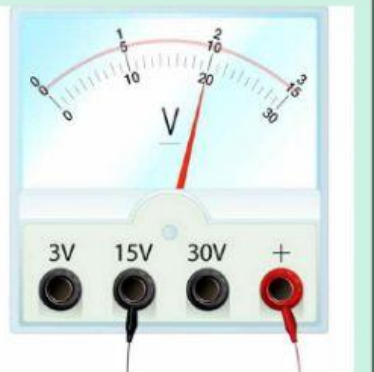		
① 2 V ② 10 V ③ 20 V	① 2 V ② 10 V ③ 20 V	① 2 V ② 10 V ③ 20 V