

UNIT 7 : ELECTRICITY

WORKSHEET 1

Label the components in the electric circuit below.

PL 1

