

**7.1** Electric Circuit

**A** Name the components found in the electrical circuit below.

SP 7.1.1

Dry cell

Bulb

Switch


Connecting wire

1.

2.

3.

4.

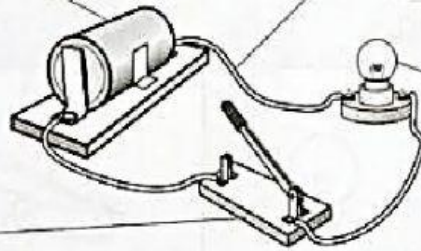

**B** Match the electrical component to its function.

Complete and break an electric circuit.

Supply electrical energy

Produce light

Connect each electrical component into a complete circuit

