



COLEGIO NUESTRA SEÑORA DEL  
ROSARIO  
BOGOTA

CLASS EXPERIENCE  
ELECTRICITY:  
SIMPLE ELECTRIC  
CIRCUIT

NAME:

GRADE:

TEACHER NAME:

DATE:


1 - Label the diagram

battery

wire

switch

bulb

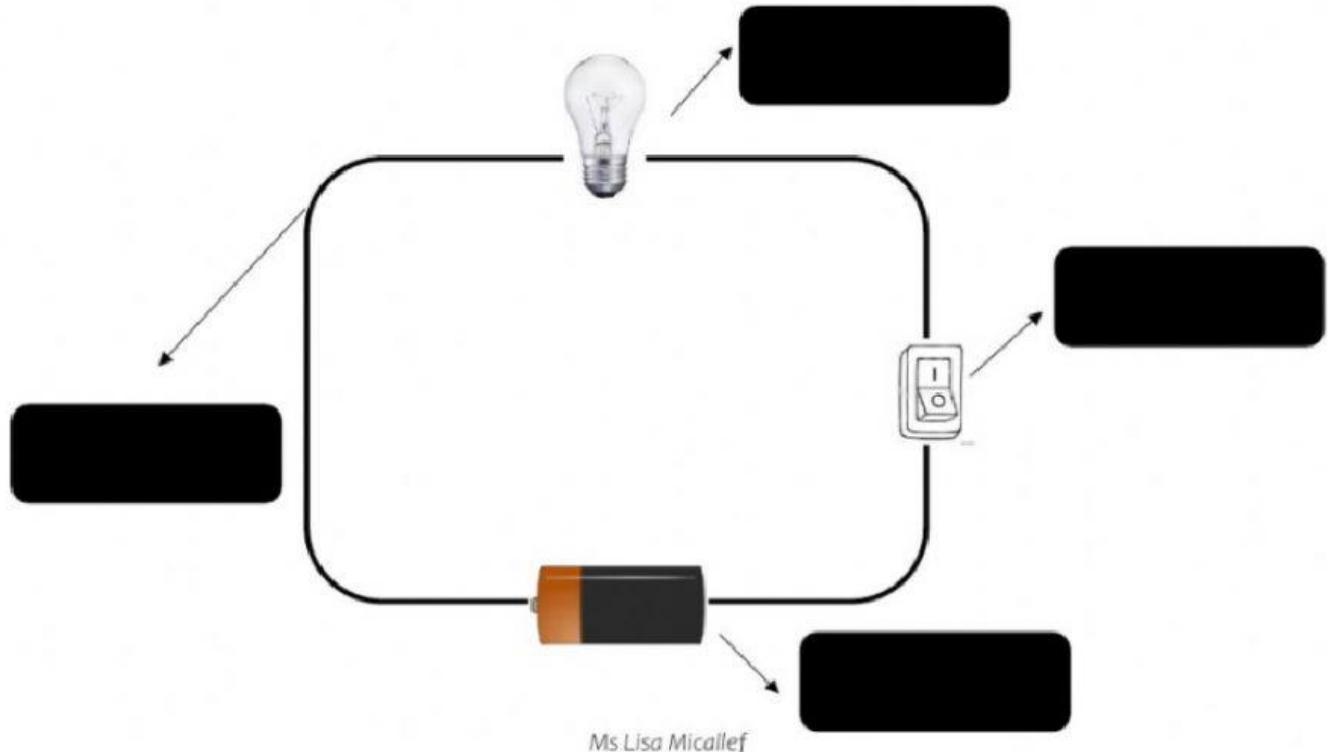

2- Write CONDUCTOR or insulator



STEEL



PLASTIC



WOOD



SILVER



COOPER



GLASS



ALUMINIUM



SALT WATER



IRON

3- What is the function of the WIRE in the electric circuit?

- A- It is a conductor allow electricity flow
- B- It is an insulator allow electricity to flow
- C- It is a conductor doesn't allow electricity to flow

4- Check those activities for which you need use electricity.



5-

