



**COLEGIO NUESTRA SEÑORA DEL  
ROSARIO  
BOGOTA**

**CLASS EXPERIENCE  
ELECTRICITY:  
SIMPLE ELECTRIC  
CIRCUIT**

**NAME:**

**GRADE:**

**TEACHER NAME:**

**DATE:**


1- Label the diagram

battery

wire

switch

bulb

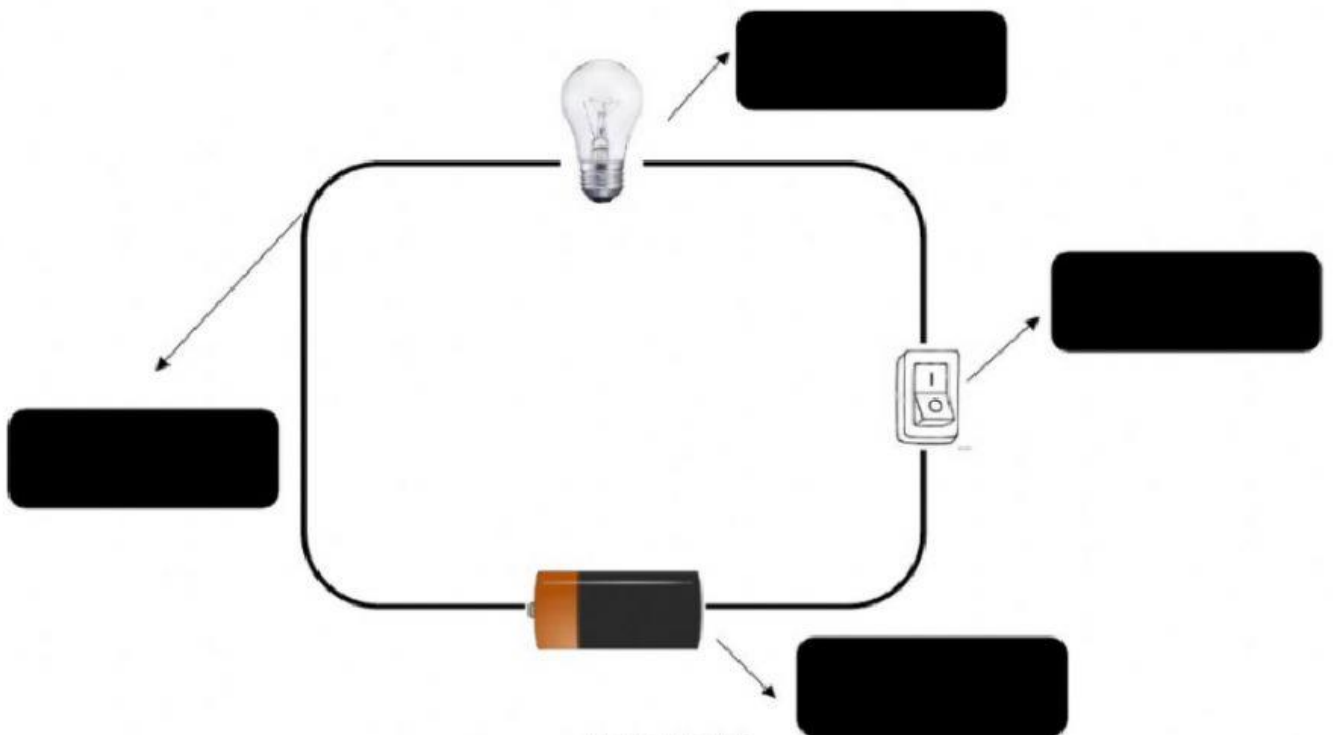

Ms Lisa Micallef

2- Write CONDUCTOR or insulator



**STEEL**



**PLASTIC**




**WOOD**



**SILVER**



**COOPER**

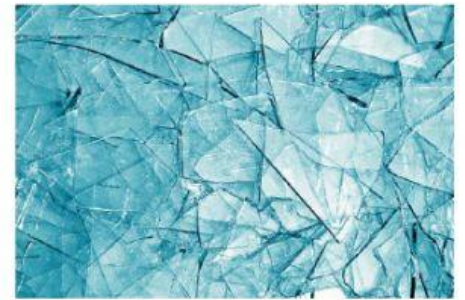

**GLASS**



**ALUMINIUM**



**SALT WATER**



**IRON**

3- What is the function of the WIRE in the electric circuit?

A- It is a conductor allow electricity flow

B- It is an insulator allow electricity to flow

C- It is a conductor doesn't allow electricity to flow

4- Check those activities for which you need use electricity.



5-



