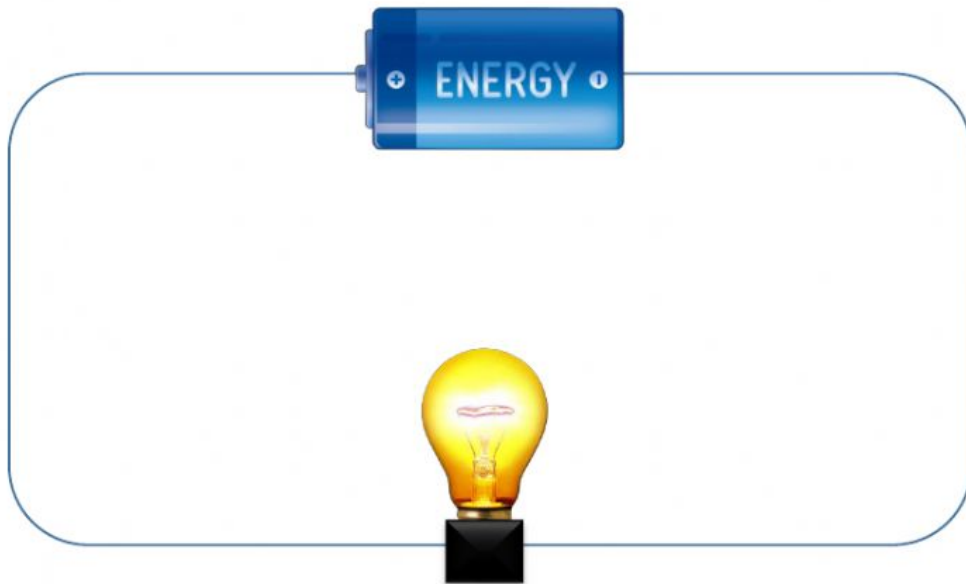


Science Year 3

Complete Circuit and Incomplete Circuit.

Read the note below carefully.



Look, at the picture carefully.

1. Do the bulb light up?


☐

2. When all the electric component are connected together

the bulb light up and this is what we call **Complete**

**Circuit.**

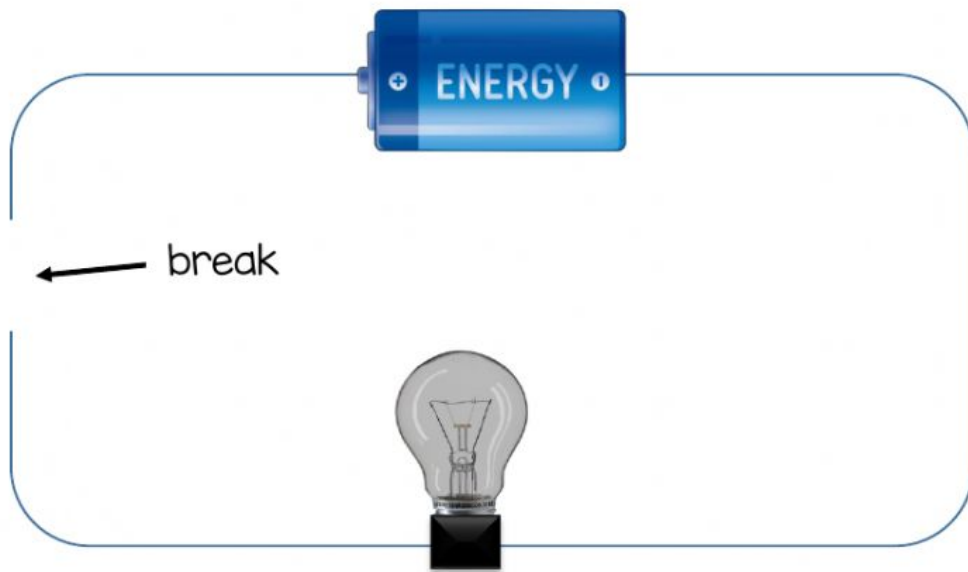3. **Complete circuit** make the bulb lights up.



Look, at the picture carefully.

1. Do the bulb light up?

☐

2. When there is a **break**, the wire are not connected. The bulb do not light up and this is what we called **Incomplete Circuit**.

3. **Incomplete circuit** do not make the bulb lights up.

Science Year 3

Choose the correct answer if it is **Complete Circuit** or **Incomplete Circuit**

