

## Electric Circuit.


### Switch.

- Look at the picture below, tick the picture that show a switch.




All of the above picture is actually a switch.

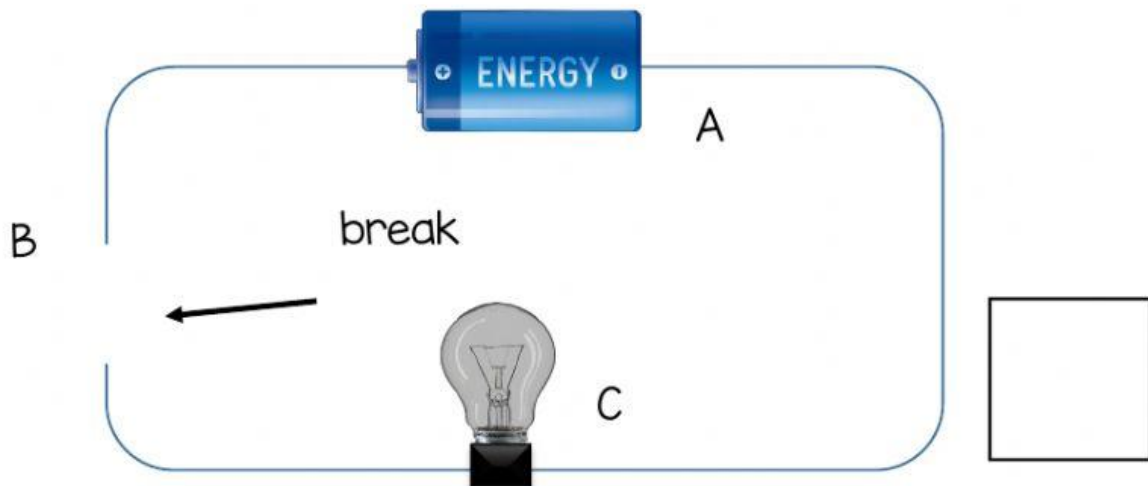- Where do you put a switch in a simple circuit?



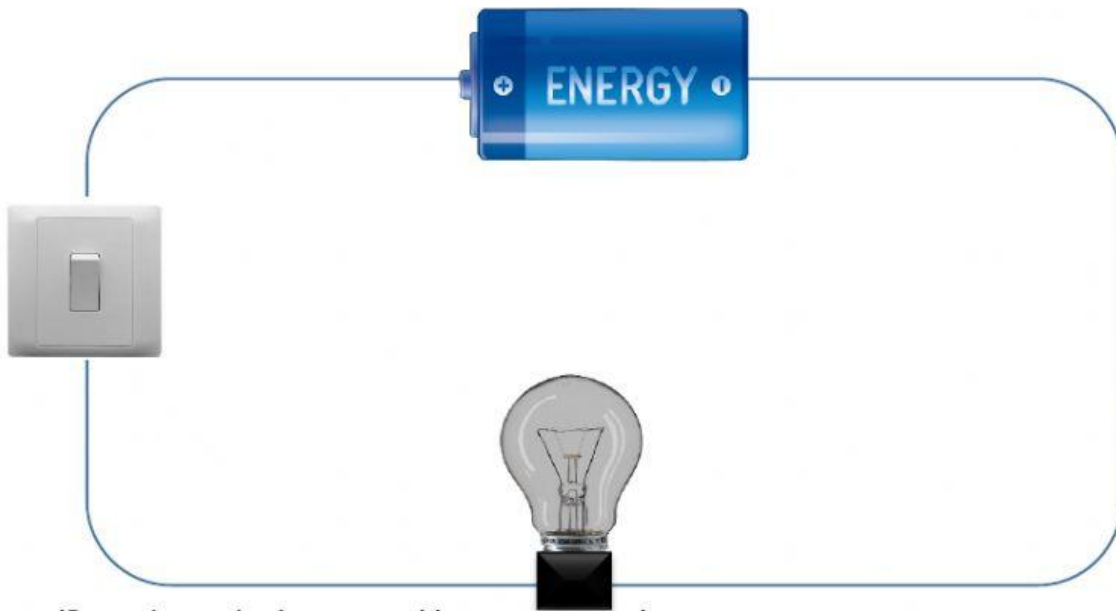What happened to the light bulb when you "Switch on" the switch?



- Read and choose the correct answer.

Conclusion:

A  is needed to turn on and turn  an electric circuit.

So what happened to a the light bulb if you switch off the electric ciruict?