



WORKSHEETS



For the Prathomsueksa 6 students of Bangkulad School

Name: _____ Room: _____ Number: _____

A. Click COMPLETE if the sentence is about a complete circuit and INCOMPLETE if the sentence is about an incomplete circuit.

1. The switch is turned on. **COMPLETE** **INCOMPLETE**

2. Electricity can not flow. **COMPLETE** **INCOMPLETE**

3. It is also called an open circuit. **COMPLETE** **INCOMPLETE**

4. The bulb lights up. **COMPLETE** **INCOMPLETE**

B. Match the words in column A to the symbols in Column B. Connect them by drawing lines.

COLUMN A

5. on switch

6. connecting wire

7. battery

8. off switch

9. bulb

10. simple electric circuit

COLUMN B

