

## Components in Electrical Circuits




**A. Complete the statements about the components of electrical circuits. Choose your answer from the box.**

1. \_\_\_\_\_ supplies energy to the electrical circuit.
2. \_\_\_\_\_ shows if electric current flows through.
3. \_\_\_\_\_ open a circuit to stop electricity flowing or close a circuit to allow electricity to flow.
4. \_\_\_\_\_ change electrical energy into mechanical energy that makes machine works.
5. \_\_\_\_\_ make a buzzing sound.

motor	switch	bulb
battery	buzzer	

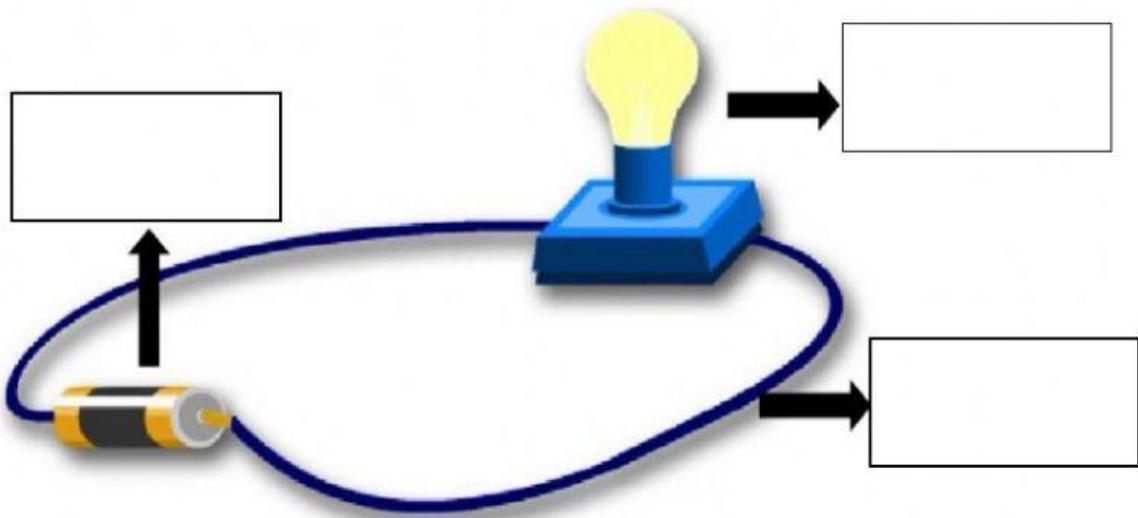**B. Label the components of an electrical circuit.**



C. Labels the component with the circuit symbols.

