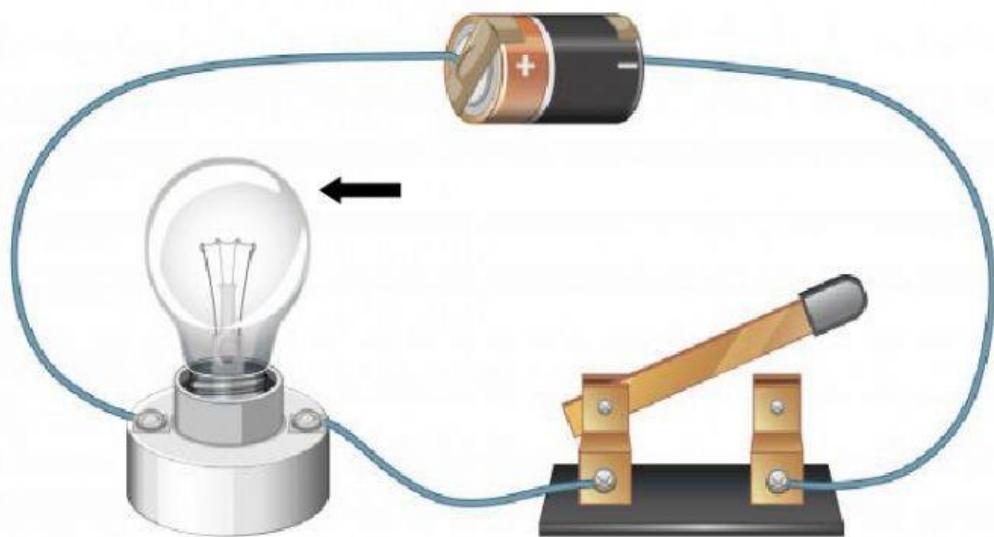


Match each word to the circuit.



|             |
|-------------|
| bulb        |
| switch      |
| wire        |
| cell        |
| bulb holder |

Match the name to the picture and the function.

wire



Turns the circuit on or off

buzzer



Moves something move

bulb



Stores the electricity

motor



Connects the parts of a circuit

cell



Lights up

switch



Makes a sound