
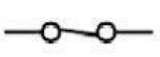
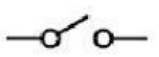
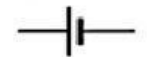


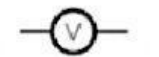


Year 2 Science
(Week 36)
Worksheet – Electric Circuits

Name: _____ Class: Year 2 A B C D Date: _____

1. Electricity flows in a circuit from the positive pole of a battery to its negative pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit.

 battery	 closed switch	 open switch	 cell	 voltmeter
 buzzer	 lamp	 lamp	 motor	 wire

Label the circuit below.

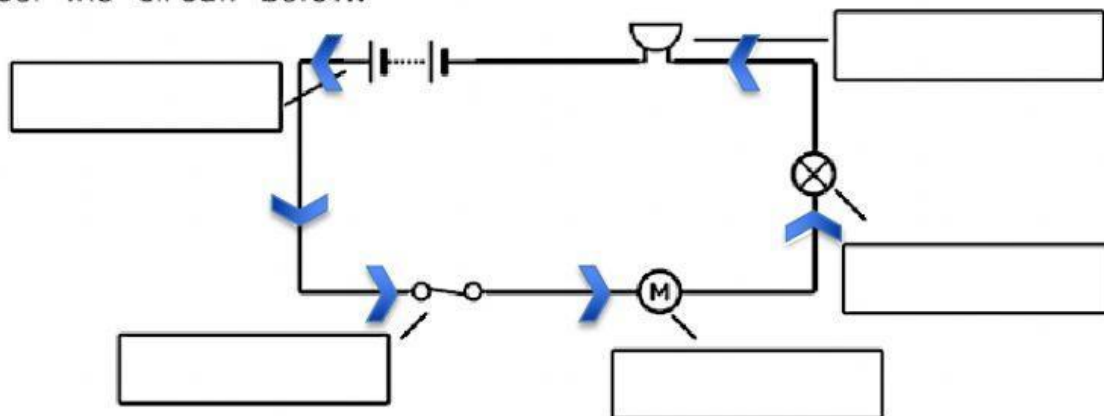

Follow the arrows to complete the sentences.

2. The electric current leaves the and travels through the It then passes through the, next through the and then lights up the and finally through the before returning to the battery.