




Name: _____

SCIENCE Class 2CI_____


Date: _____

Topic: Unit 5.3 Making a Circuit



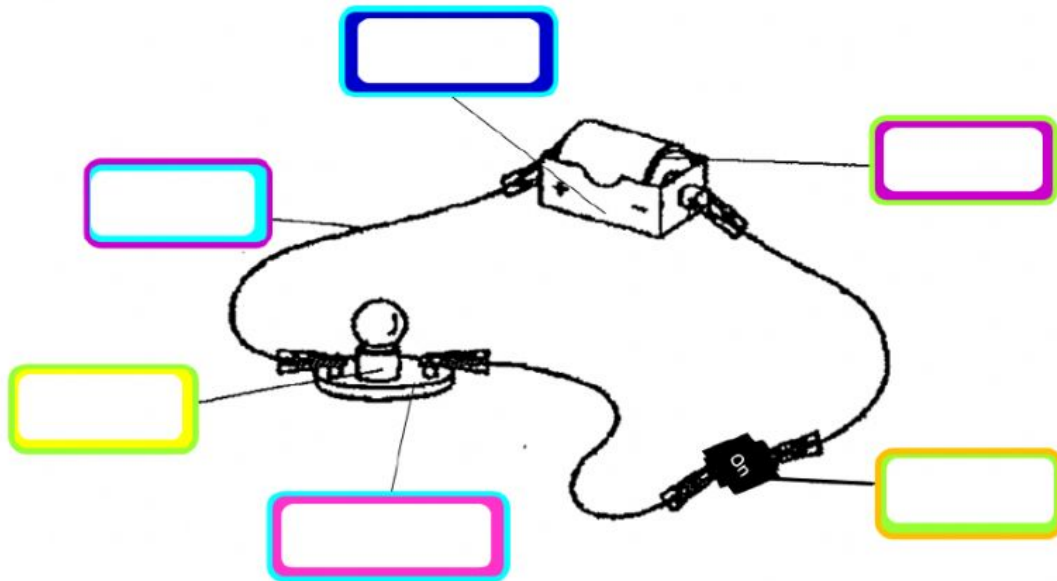
1. Look at circuit below and label its components.






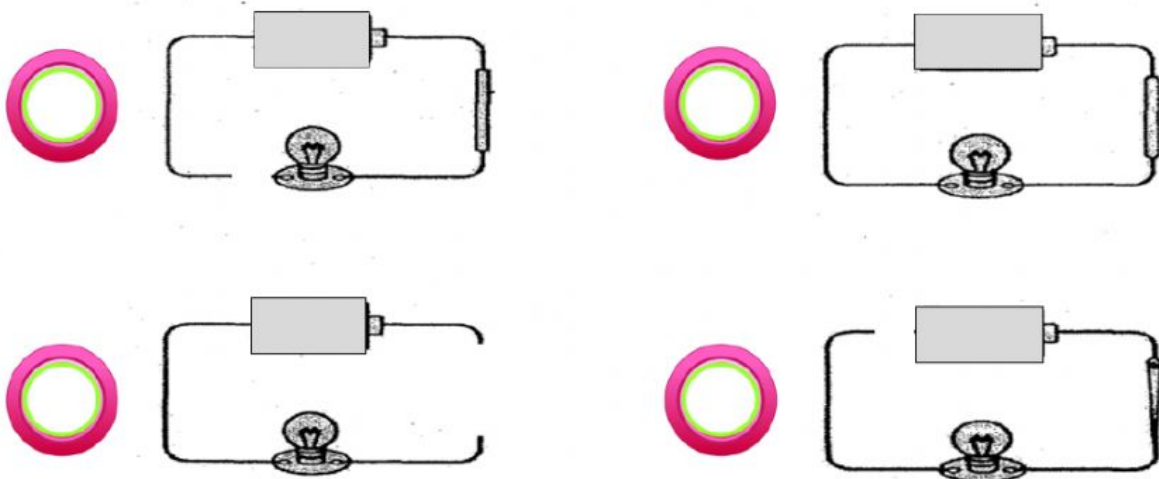
2. Which of the following bulbs **will not light up**?



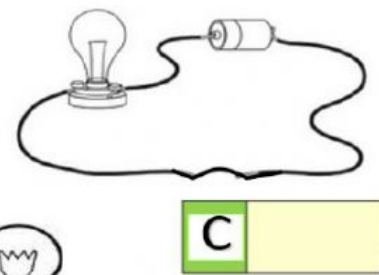
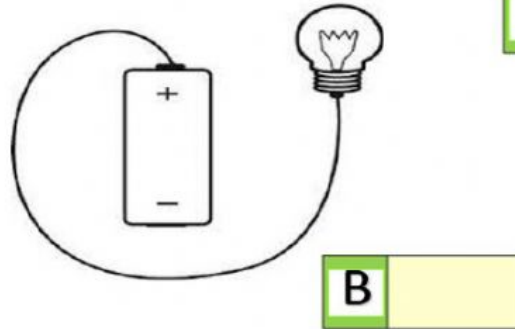
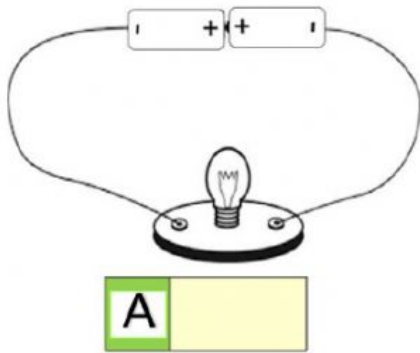
3. In which circuit will the bulb light up?



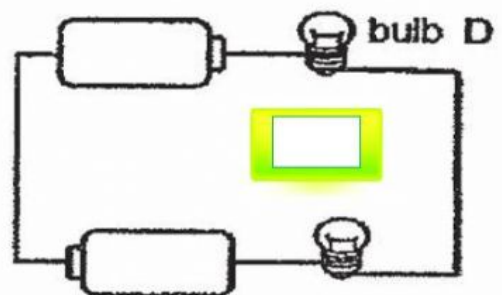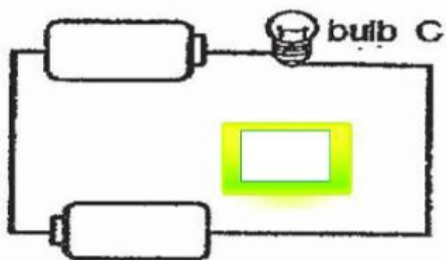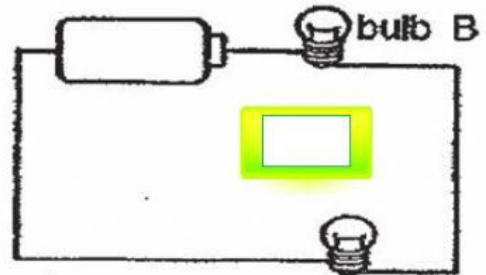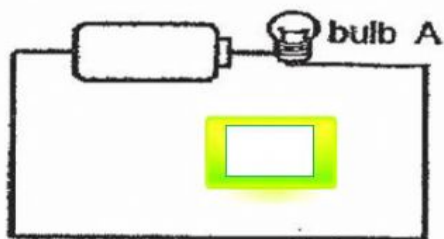4. Study the four circuits below carefully.
Which of the bulbs have the **same brightness**?



5. Look at circuit X, Y and Z.

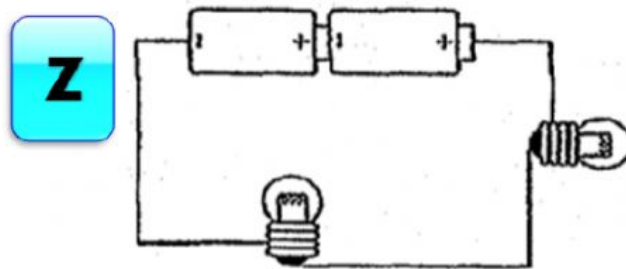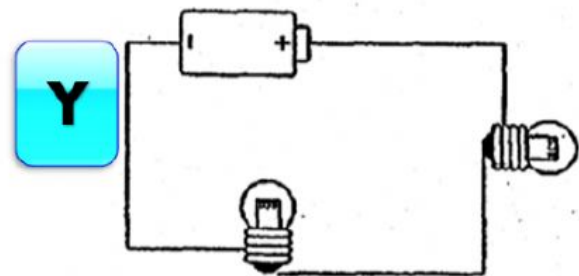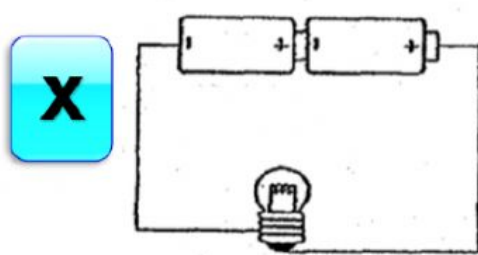

Put the circuits in order according to the brightness of the bulb.

