

Electrical Circuits

Tell whether the light bulb or bulbs will light or will not light based on the circuit.

1.

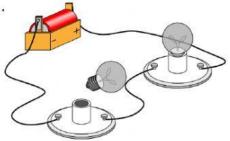

2.

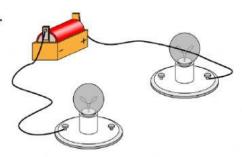

3.

