

Write True or False

1. A buzzer makes noise.
2. A switch turns the circuit on and off.
3. A motor makes light.
4. The wires connect the parts of a circuit.
5. The circuit will work if there is a gap.
6. Mains electricity is safer than cell electricity.
7. The cell stores electricity.
8. A bulb makes something move.

Does it use electricity?

