

Chapter1: Circuit construction

Label the figure below using the words below:

Name:

push button

load

voltage source

wires

