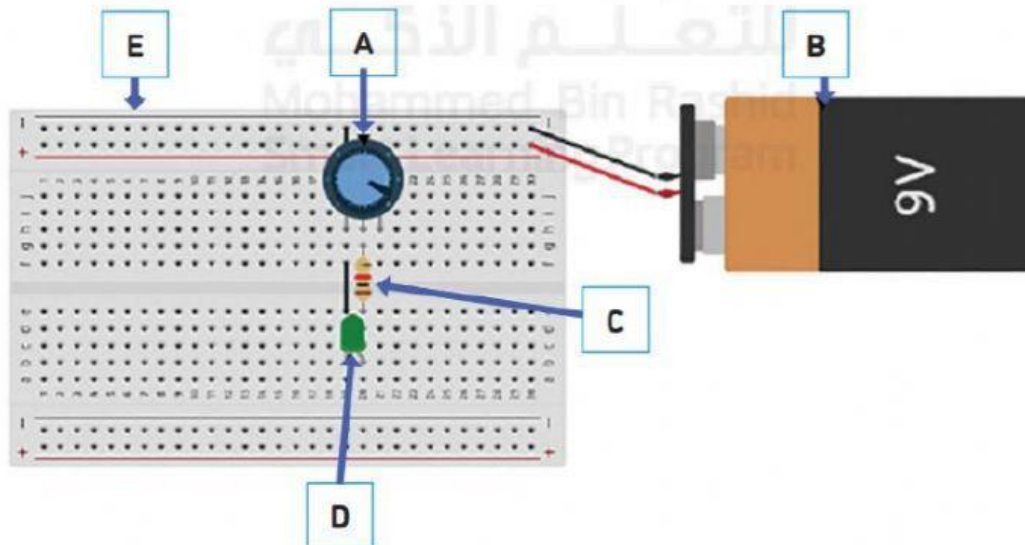


Revision : Circuit constructions:

Name: _____

'Study the electric circuit given below and then answer the questions below.'




Resistor

LED

Potentiometer

Battery

Breadboard

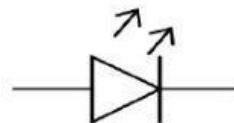

1. Complete the table below about the given circuit diagram.

Label	Component name	Schematic symbol
A		
B		
C		
D		
E		