

Revision : Circuit constructions:

Activity 1.1.7

Name: _____

Which of the following schematic diagrams represents the circuit shown below?

