

Date: _____

SCIENCE YEAR 6

TOPIC: ELECTRICITY

ELECTRIC CIRCUITS

1. Name the components below.



2. What happens to the electricity when the circuit is **complete**?

When the circuit is complete, electricity from one end of the cell, through the and the , to the other end of the cell. This circuit is also called

3. What happens to the electricity when the circuit is **incomplete**?

When the circuit is incomplete, electricity flow through the wires. The bulb light up. This circuit is also called