



Activity 7




Look at the two circuits below. Which one is series, and which one is parallel?

Circuit 1



- Series Circuit
- Parallel Circuit

Circuit 2

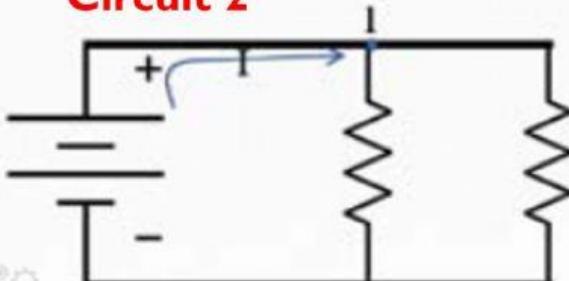

- Series Circuit
- Parallel Circuit

What will happen to the current when it reaches point (1) in Circuit 2?

- the current will be distributed over the paths.
It will have two ways to flow
- the current will be in one path.
It will have one way to flow
- Nothings will happen .