

End of unit quiz




Activity 15



What have you learned? Do the quiz.

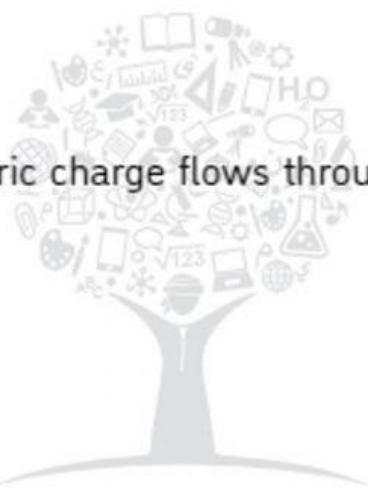1. An electronic component that resists the flow of current in an electric circuit is called
 - circuit
 - resistor
2. The rate at which electric charge flows through a certain point is called
 - voltage
 - current
 - capacitor
 - thermistor
3. R_{total} for a series circuit is equal to the addition of the resistance of all the resistors.
 - True
 - False
4. Ohm's Law explains the relationship between voltage, current and resistance.
 - True
 - False
5. In parallel circuits, electric current has more than one path
 - True
 - False



برمجة موزع بن راشد
Smart Learning Program