

End of unit quiz




Activity 15



What have you learned? Do the quiz.

- An electronic component that resists the flow of current in an electric circuit is called.....
 - circuit
 - resistor
- The rate at which electric charge flows through a certain point is called.....
 - voltage
 - current
 - capacitor
 - thermistor
- R_{total} for a series circuit is equal to the addition of the resistance of all the resistors.
 - True
 - False
- Ohm's Law explains the relationship between voltage, current and resistance.
 - True
 - False
- In parallel circuits, electric current has more than one path
 - True
 - False

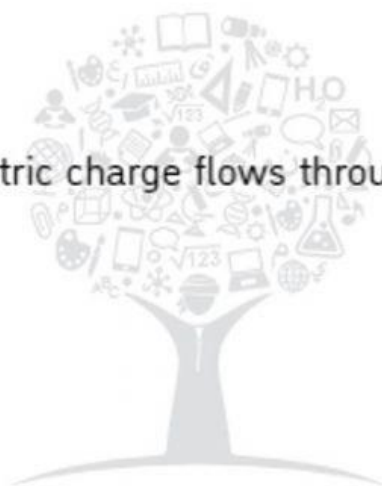

برنامج محمد بن راشد
للتنمية الذكية
Mohammed Bin Rashid
Smart Learning Program

