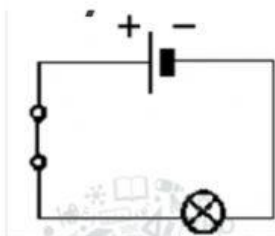



Name : _____ Grade: _____

Activity 9 : Look at the circuit carefully and answer whether the light bulb will be On or Off




Bulb ON

Bulb OFF

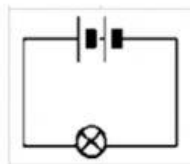


Bulb ON

Bulb OFF

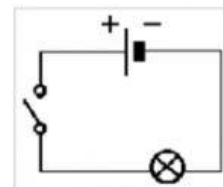


Bulb ON

Bulb OFF

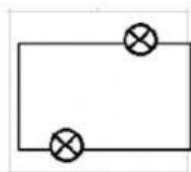


Bulb ON

Bulb OFF

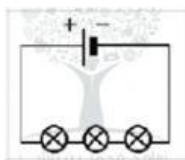

Bulb ON

Bulb OFF

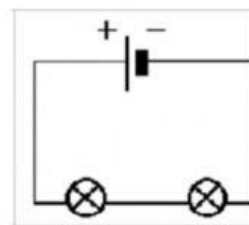

Bulb ON

Bulb OFF