



Activity 9



Look at these circuit diagrams. Which will work? Which need repairs?

Bulb On Bulb Off	Bulb On Bulb Off	Bulb On Bulb Off
Bulb On Bulb Off	Bulb On Bulb Off	Bulb On Bulb Off
Bulb On Bulb Off	Bulb On Bulb Off	Bulb On Bulb Off