

Activity 6

Circuit drawings

1 Draw the symbols for each component. Write the name of each symbol.

Component

Symbol

(a)



(b)



(c)





Component

Symbol


(d)



(e)

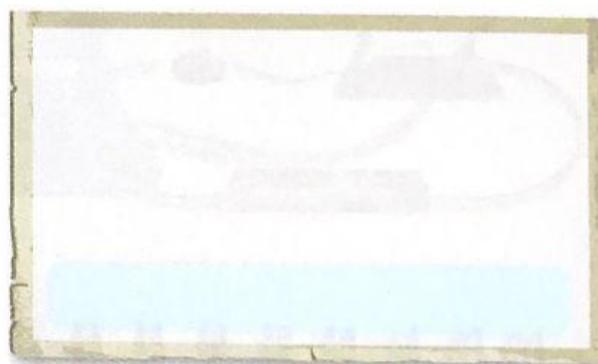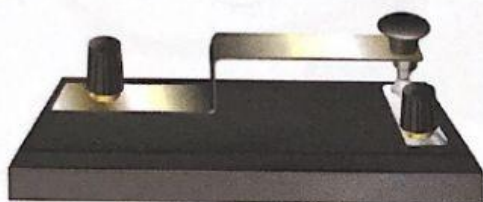

(f)

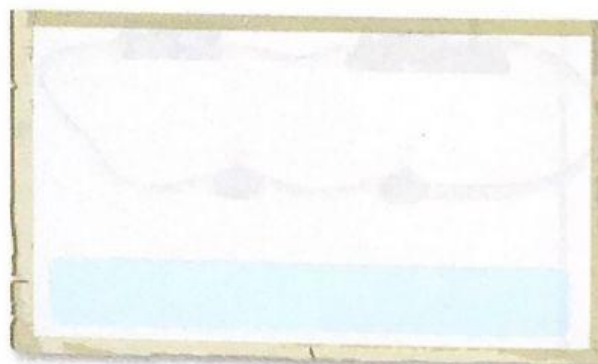

(g)

