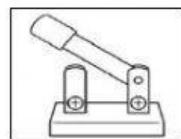


ELECTRIC CIRCUITS (ASSESSMENT SHEET)


1. Observe the electrical components below.



a) Drag and match the component to its function correctly below. [3]
 b) Name the electrical components. [3]

Function	Electrical component
Supply (produce) electrical energy	<input type="text"/>
Open and close a circuit	<input type="text"/>
Produce light	<input type="text"/>

2. Observe the circuits below.

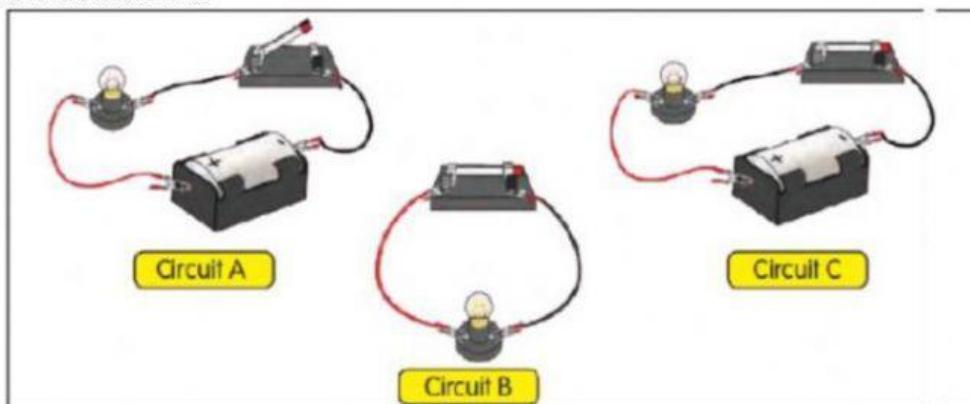

a) In which circuit will the bulb light up? Circuit _____ [1]
 b) Why does the bulb light up? Because the circuit is _____. [1]
 c) In which circuit(s) will the bulb **not** light up? Circuit _____ [1]
 d) Why does the bulb not light up? Because the circuit is _____. [1]

3. Complete the two statements below by filling in the blanks. [6]

(i) In a _____ or _____ circuit, the bulb will light up because electricity _____ through the circuit.

(ii) In an _____ or _____ circuit, the bulb will **not** light up because electricity _____ through the circuit.