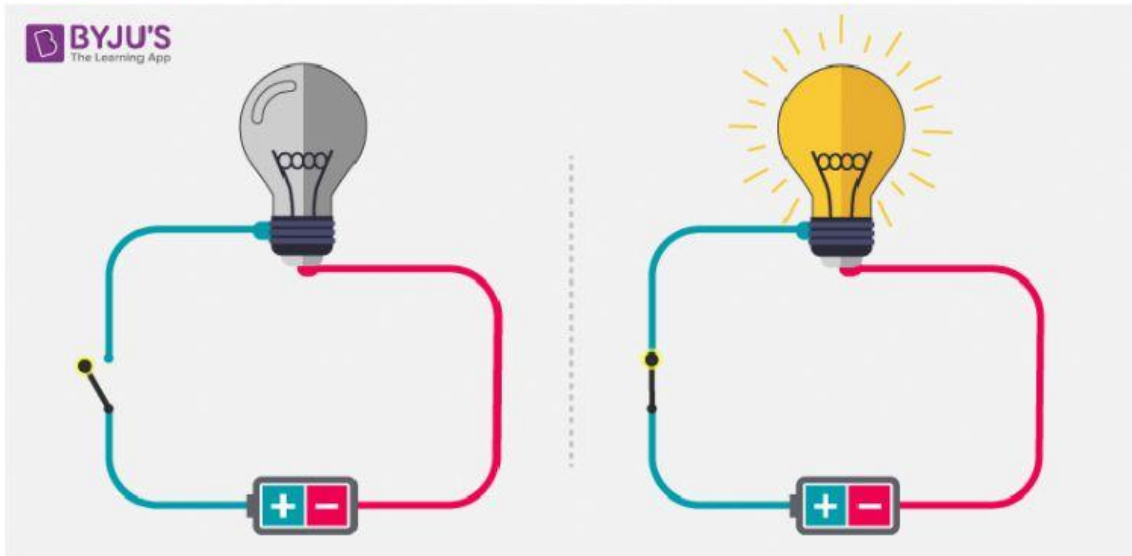


Name: _____

Date: _____

Electric circuit



Circuit A

Circuit B

- 1. Which of the circuit above is a complete circuit?**

- 2. What do you think will happen if the circuit is complete? Give reason.**