

Name: _____

Date: _____

Electric circuit

Answer the following questions.

1. Write down **three basic components** of an electric circuit.

a. _____

b. _____

c. _____

2. Dry cell is a _____ of electricity.

3. A switch is used to _____ or _____ an electric circuit.

4. The bulb will light up if the circuit is _____.

5. The bulb will not light up if the circuit is _____.