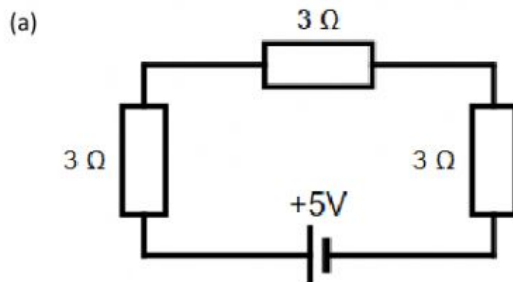


Name: (Yr)


Date:

Exercises: Effective Resistance


1. For each circuit calculate the current out from the cell.




Current: Unit:

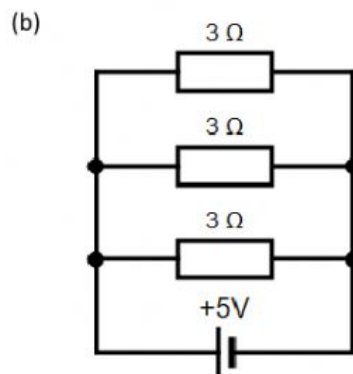


Current: Unit:

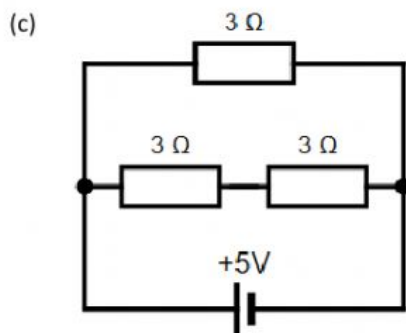


Current: Unit:

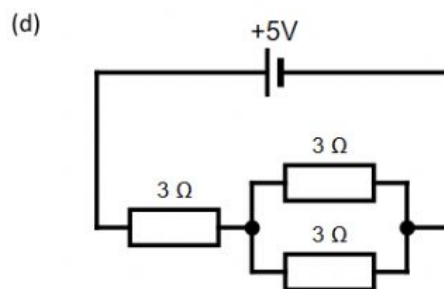

Current: Unit:

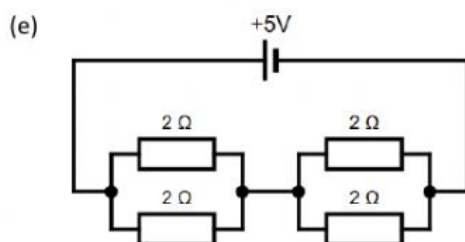

Current: Unit:

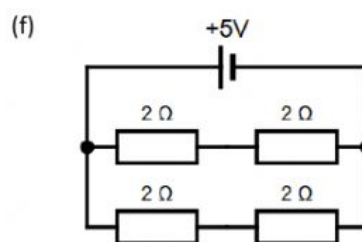

Current: Unit: