


Name: (Yr)

Date:.....


Exercises: Effective Resistance

1. Calculate the effective resistance for each circuit.

(a)

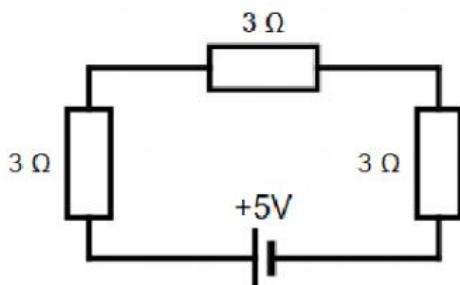


(b)

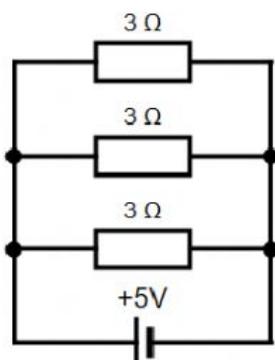


Effective resistance =

Effective resistance =

(c)

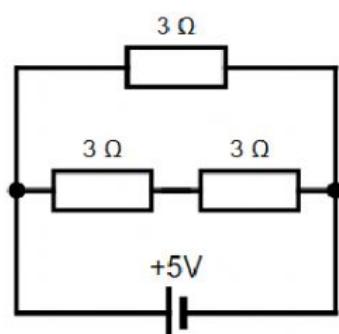


(d)

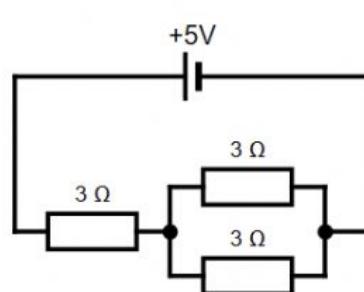


Effective resistance =

Effective resistance =

(e)

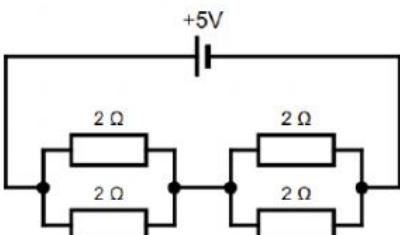

(f)

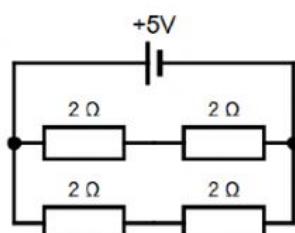

Effective resistance =

Effective resistance =