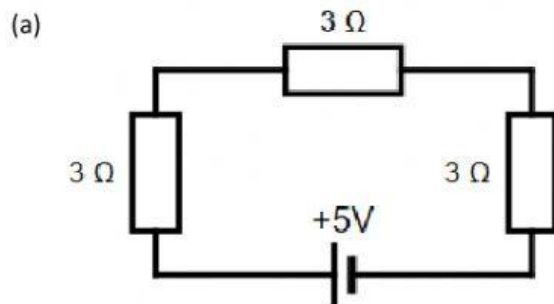


Name: (Yr)


Date:.....

Exercises: Effective Resistance


1. Calculate the effective resistance for each circuit.




Effective resistance =

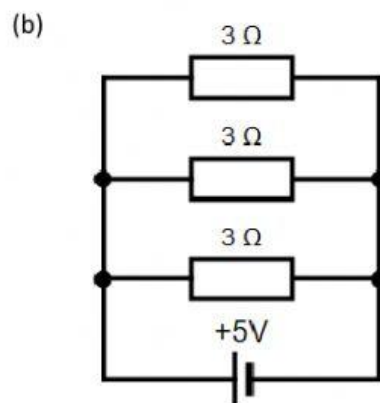


Effective resistance =

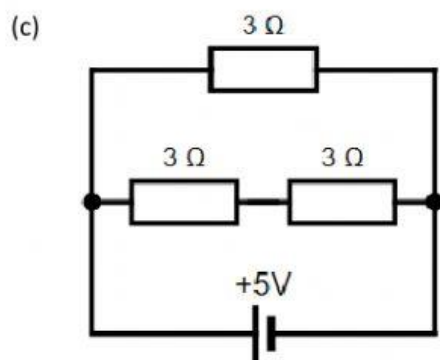


Effective resistance =

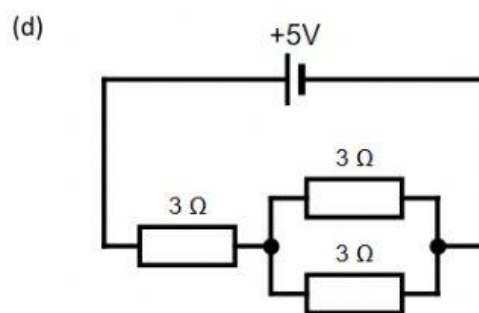

Effective resistance =

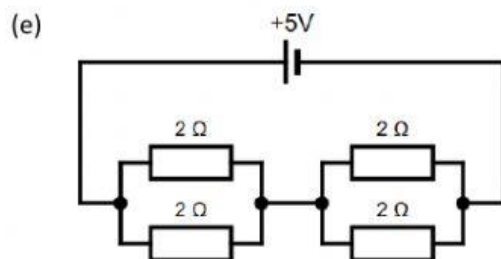

Effective resistance =

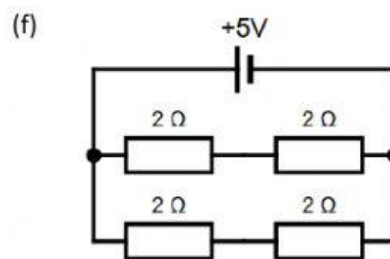

Effective resistance =