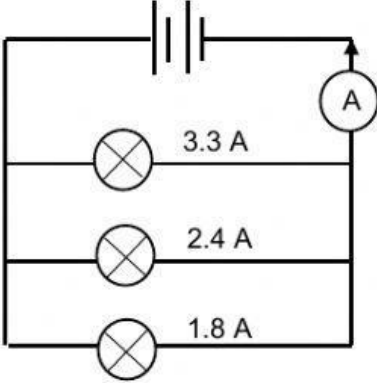


Name: () Class: Date:

LIVE Assignment 2: AMMETER READING

	Circuit Diagram	Ammeter reading
(a)		
(b)		
(c)		

	Circuit Diagram	Ammeter reading
(d)		
(e)	* please note that the two light bulbs are identical. 