

电线	•		•		•		•	连接元件
蜂鸣器	•		•		•		•	接通或截 断电路
干电池	•		•		•		•	提供电流
开关	•		•		•		•	发出声音