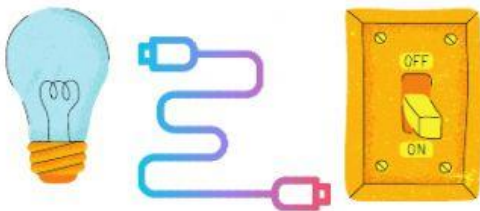


Put in order the steps of the experiment of the electrical circuit.

Connect a cable to the bottom of the light bulb and connect it to the switch.



EXPERIMENT

Connect one cable to the battery.



QUESTIONS


- **How can you connect all the parts?**
- **How can you turn the light bulb on?**



Screw the light bulb in the bulb holder.



Connect a cable to the bulb holder.

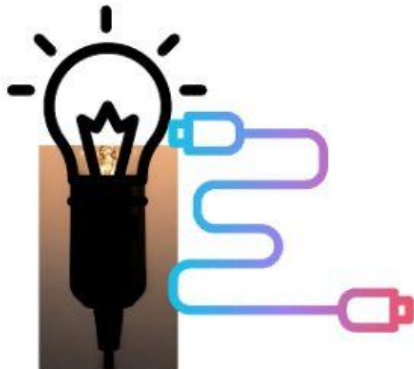

OBSERVATIONS

We have many materials:

- A battery
- A light bulb
- A holder
- Scissors
- Three cables



Turn the light bulb on and off.



Use a cable to connect the switch to the battery.

