

Total resistance



Activity 11

Theory



Calculate the total resistance of these resistors combination.



R =

Ω

S

T

R

E

A

M

T