



Activity 5



Look at the circuit below. Draw arrows to indicate the flow of the electric current. Start from the positive terminal of the power source.

Note that this simple circuit has:

- ⊙ a battery - DC electrical source
- ⊙ a light bulb – load
- ⊙ electric wires - conductive path

