

c) Calculate the voltage across each resistor using Ohm's law.

Power Supply Voltage	Resistor value	Using the multimeter		Using Ohm's law
		Current value	Voltage value	Voltage value
9 V	330Ω			
	500Ω			

d) Can you observe any pattern in the voltage value when the resistor's value increases?

برنامج محمد بن راشد
للتعلم الذكي
Mohammed Bin Rashid
Smart Learning Program