
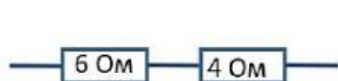


Прізвище, клас

Знайдіть загальний опір кола

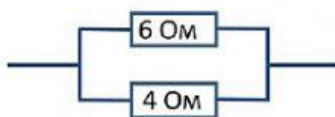


$$R_{\text{заг}} = \quad \text{Ом}$$




$$R_{\text{заг}} = \quad \text{Ом}$$




$$R_{\text{заг}} = \quad \text{Ом}$$

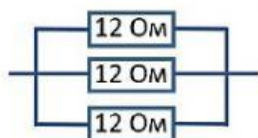


$$R_{\text{заг}} = \quad \text{Ом}$$

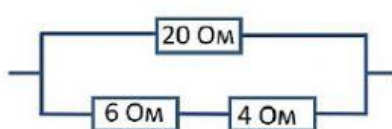


$$R_{\text{заг}} = \quad \text{Ом}$$

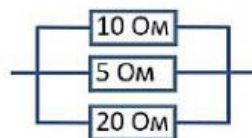


$$R_{\text{заг}} = \quad \text{Ом}$$

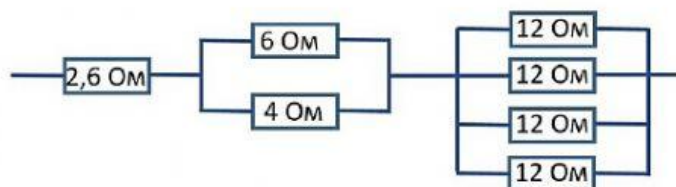


$$R_{\text{заг}} = \quad \text{Ом}$$

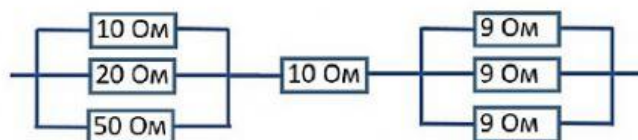

$$R_{\text{заг}} = \quad \text{Ом}$$

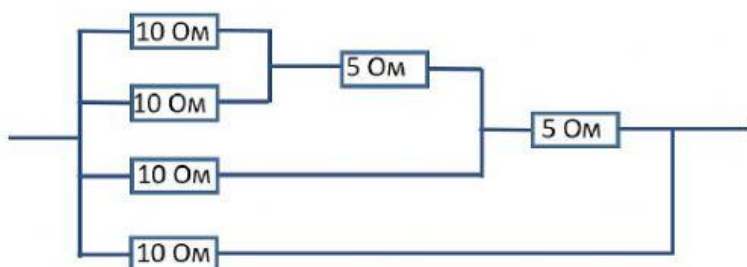

$$R_{\text{заг}} = \quad \text{Ом}$$

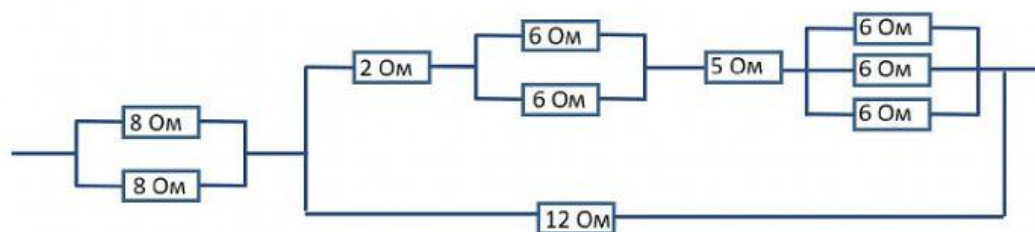

$$R_{\text{заг}} = \quad \text{Ом}$$