
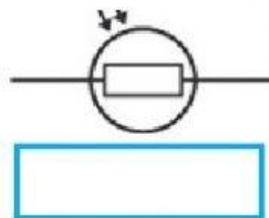
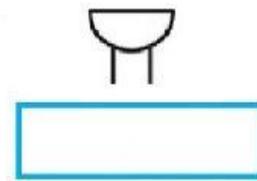
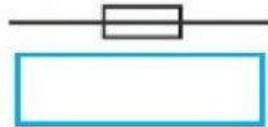
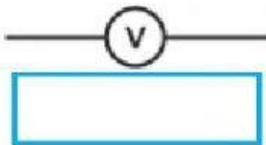
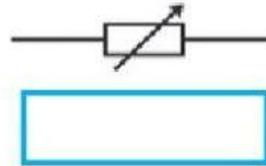
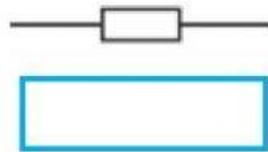
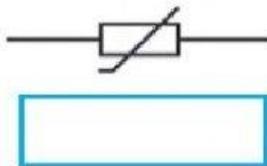
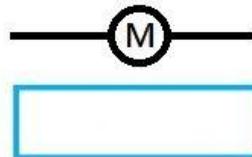
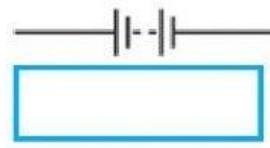
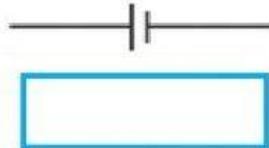
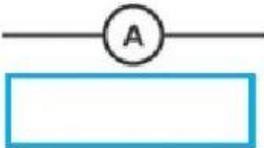
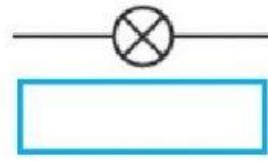
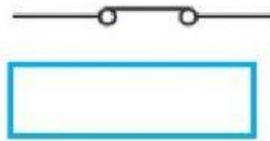


Components of Electric Circuits

Name: _____ Class: _____ Date: _____

Circuit Symbols

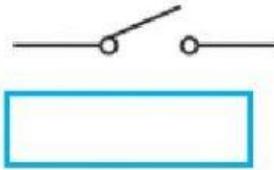Use the components' names given below and write them underneath their symbol.



motor

buzzer

open switch

battery

fuse

ammeter

cell

voltmeter

variable resistor

thermistor

closed switch

LDR

resistor

lamp