

ELECTRIC CIRCUIT

Classify the components of a circuit.

Name of the component	Switch	Generator	Electric cord	Receptor
Symbol				
Definition				



It opens and closes the circuit.

It changes the electric energy into other form of energy.



Cables with wires inside that conduct electricity.

Source of energy that gives electric energy to the circuit.

