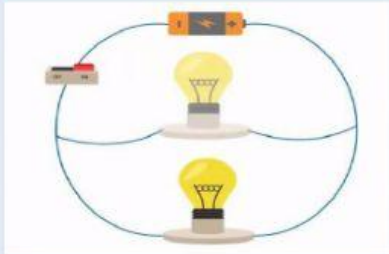


KENDRIYA VIDYALAYA KANNUR
LIVE WORKSHEET – TYPES OF CIRCUITS

NAME:


CLASS:

Drag & Drop



AN EXAMPLE FOR
SERIES CIRCUIT IS

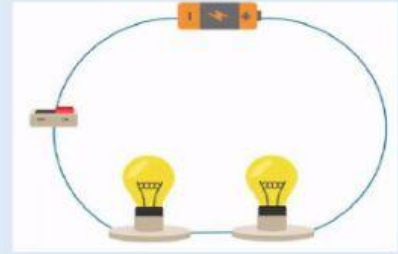IN A PARALLEL CIRCUIT,
ALL THE ELECTRICAL
COMPONENTS ARE
CONNECTED ON AFTER
ANOTHER IN A
_____ LOOP



AN EXAMPLE FOR
PARALLEL CIRCUIT IS

IN A SERIES CIRCUIT,
ALL THE ELECTRICAL
COMPONENTS ARE
CONNECTED ON AFTER
ANOTHER IN A
_____ LOOP

DECORATION LIGHTS

SERIES CIRCUIT

TWO OR MORE

SINGLE

PARALLEL CIRCUIT

HOUSE WIRING