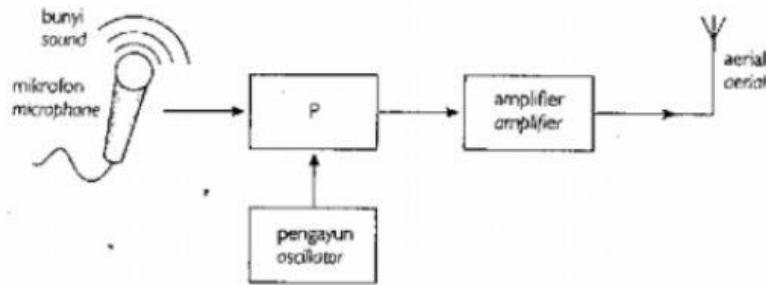


- 3 Rajah 3 menunjukkan rajah blok bagi sistem pemancar radio.  
Diagram 3 shows a block diagram for a radio transmission system.



RAJAH 3/DIAGRAM 3

- (a) Apakah fungsi setiap bahagian yang berikut?  
What is the function of each of the following parts?

i. Mikrofon/Microphone

---

ii. Pengayun/Oscillator

---

[2 markah/2 marks]

- (b) Namakan komponen yang berlabel P.  
Name the component labelled P.

---

[1 markah/1 mark]

- (c) Apakah fungsi P?  
What is the function of P?

---

[1 markah/1 mark]

- (d) Namakan **satu** komponen elektronik yang terdapat dalam amplifier dan nyatakan fungsinya.  
Name one electronic component found in the amplifier and state its function.

Komponen elektronik:

Electronic component:

---

Fungsi:

Function:

---

[2 markah/2 marks]