

Electric Circuits



Label the diagram.

battery

wire

switch

bulb

