

CIRCUIT SYMBOLS

Match the circuit symbols to the components of the circuit and identify the components

