

Worksheet time!



Name the circuit below by filling in the blanks with **complete** or **incomplete**.

