

COLEGIO BRITÁNICO INTERNACIONAL

Group	: 7 th	Academic Year	: 2023-2024
Teacher	: Eng. Diana Vaca	Date	: _____ 2023
Student's Name	: _____	Total	: _____



1. Choose if the following drawings represent series o parallel circuits:

