

Name

## Lets make electric circuits

What is an electric circuit?


A ..... which allows to flow an ..... through it, is known as .....

electric circuit

system

electric current

### Components of an electric circuit

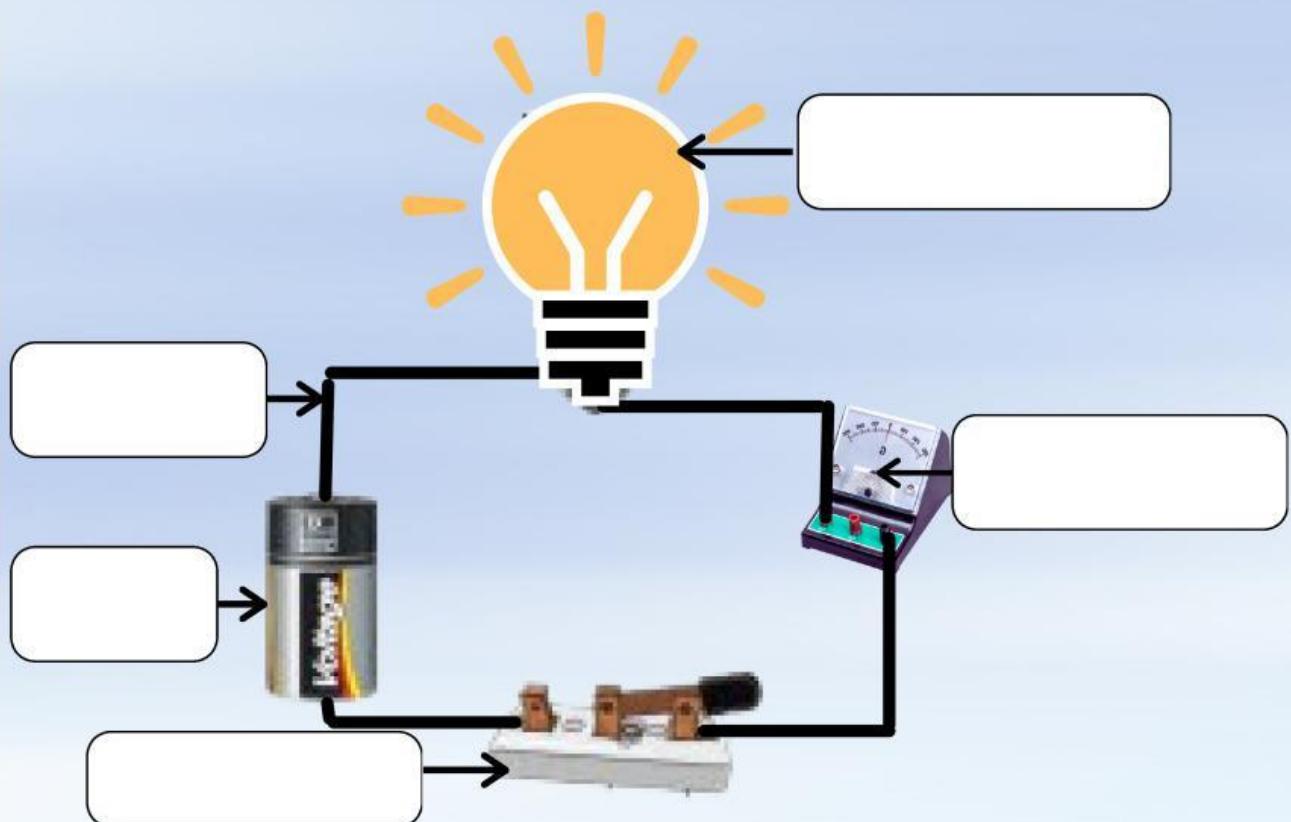

Wire



Bulb

Galvanometer

Dry cell

Switch

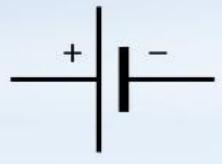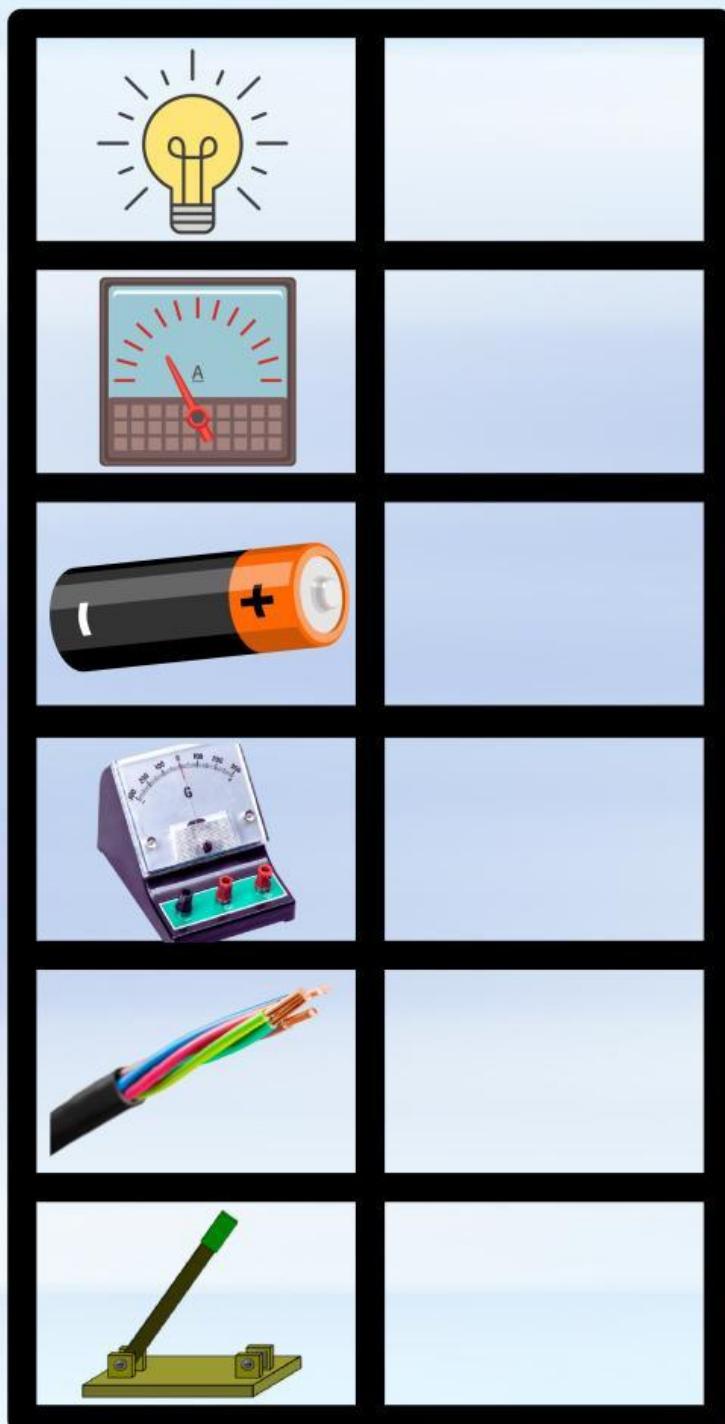Drag and drop the correct symbol of each component to the correct box



## Match the electric circuits to the correct circuit diagrams

