

A battery is an example of a _____.

What in a circuit uses electricity? _____.

What connects the power source to the load? _____.

What is the picture below called? _____.

load power source conductor series circuit

