

ELECTRONIC CIRCUIT

Write the words under the pictures.

switch / battery / wire / light bulb



.....



.....




.....



.....

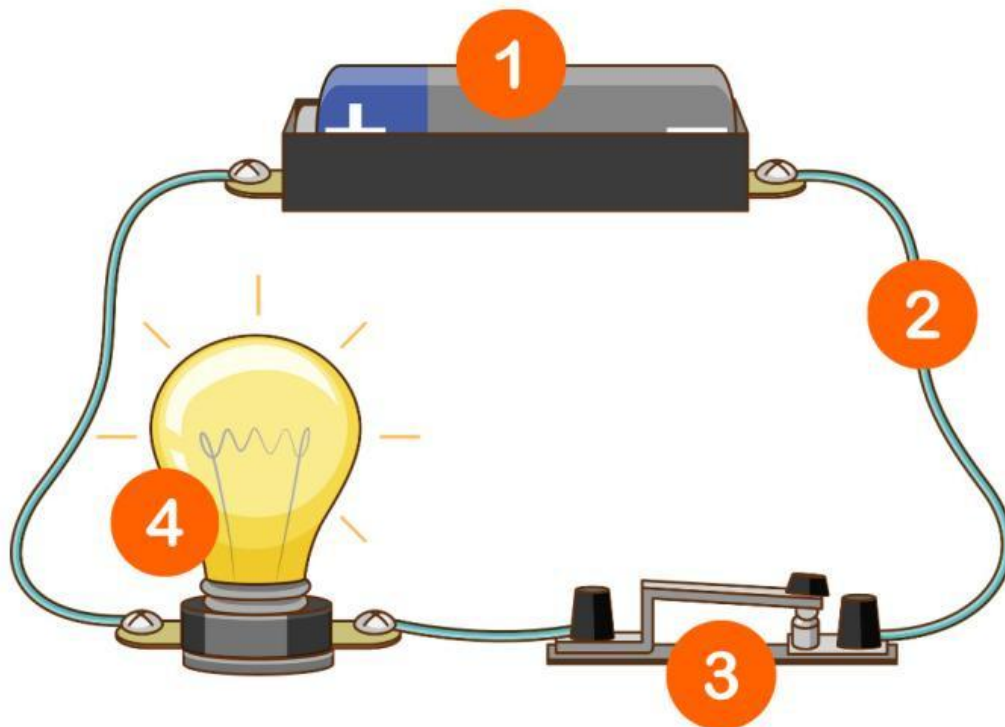Write the components of the electronic circuit below.



- 1-
- 2-
- 3-
- 4-