



CIRCUIT PARTS

Match the words with the pictures.

Closed
Switch

Light Bulb


Open
Switch

Battery



IT WORKS OR NOT?


Circle yes or no if it works

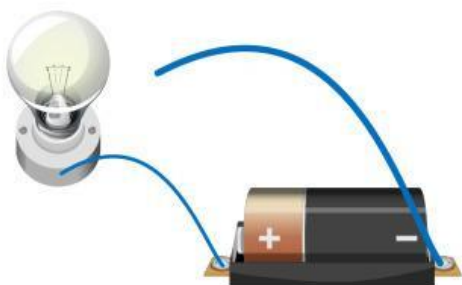


YES / NO



YES / NO

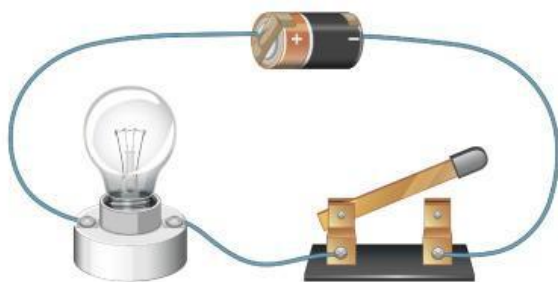

YES / NO

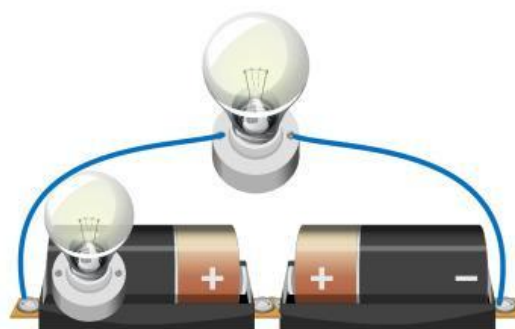

YES / NO